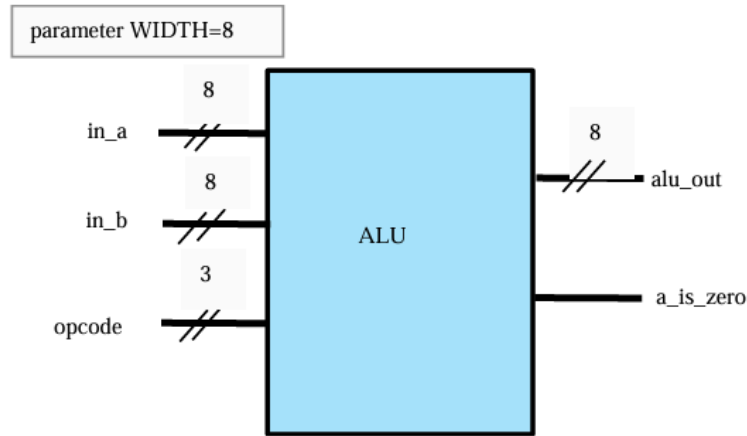


Lab 2: Modeling the Arithmetic Logic Unit

ALU performs arithmetic operations on numbers depending upon the operation encoded in the instruction. This ALU will perform 8 operations on the 8-bit inputs (see table in the *Specification*) and generate an 8-bit output and single-bit output.

In this lab, you create an ALU design as per the specification and verify it using the provided testbench. Please make sure to use the same variable name as the ones shown in block diagrams.



ALU wave form results:

